
Lab 8


Grace Dreiling


wiring

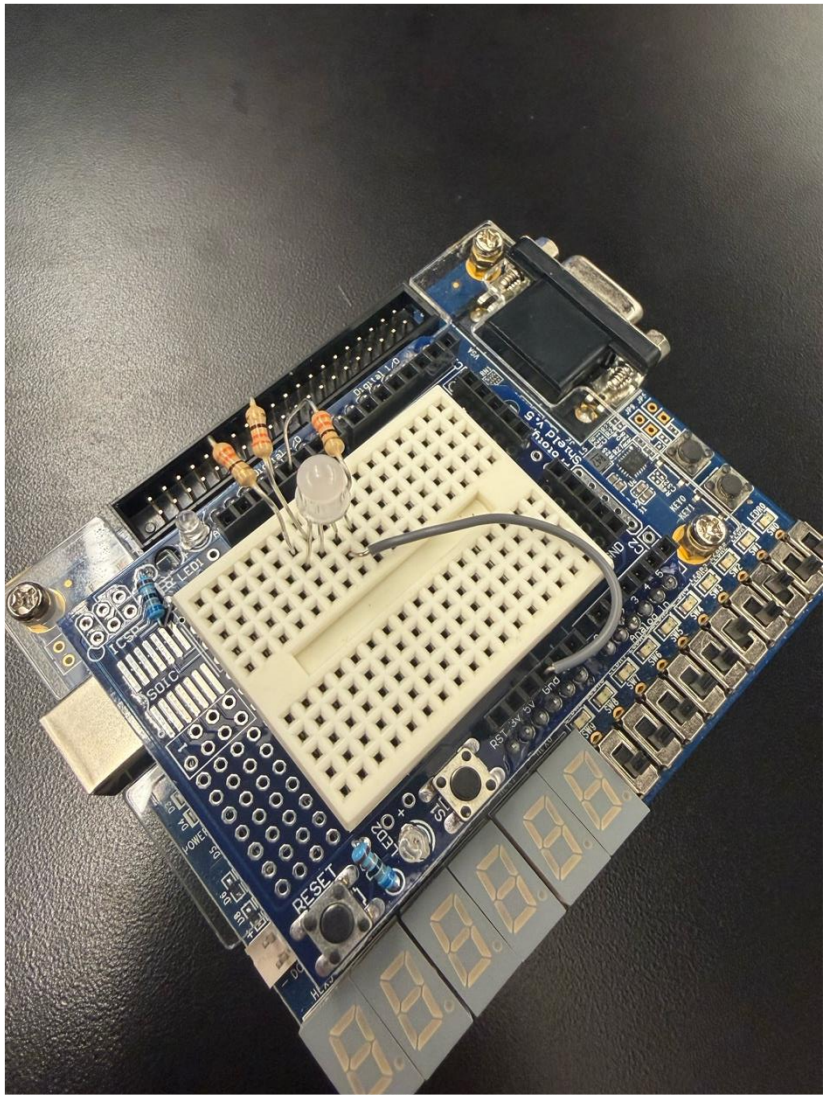3 resistors connected to red, yellow, green LEDs with ground pin connected to ground.



Thinking Process

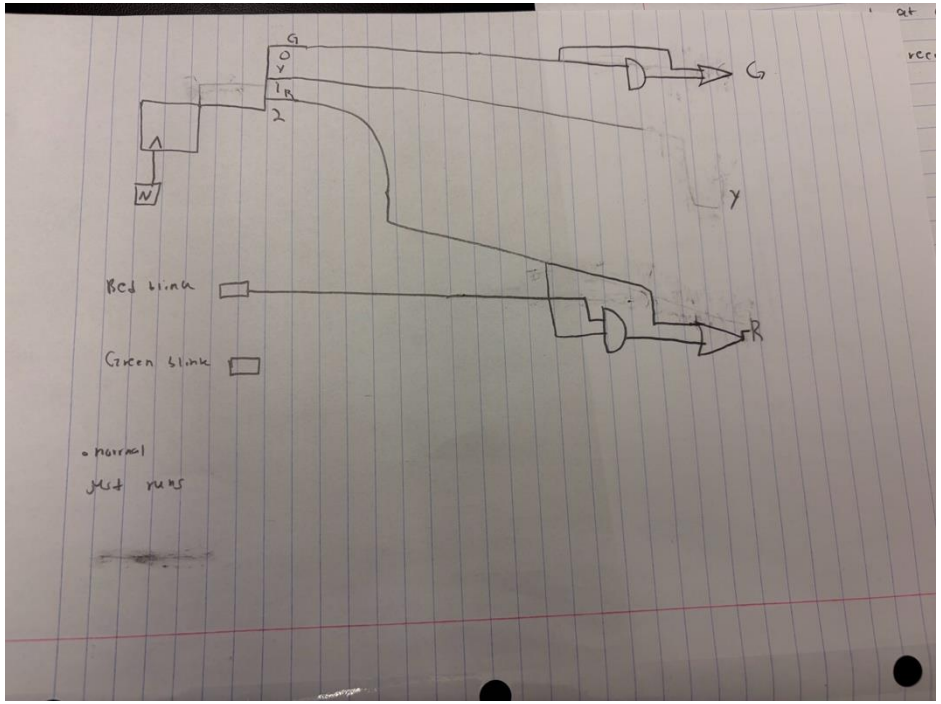


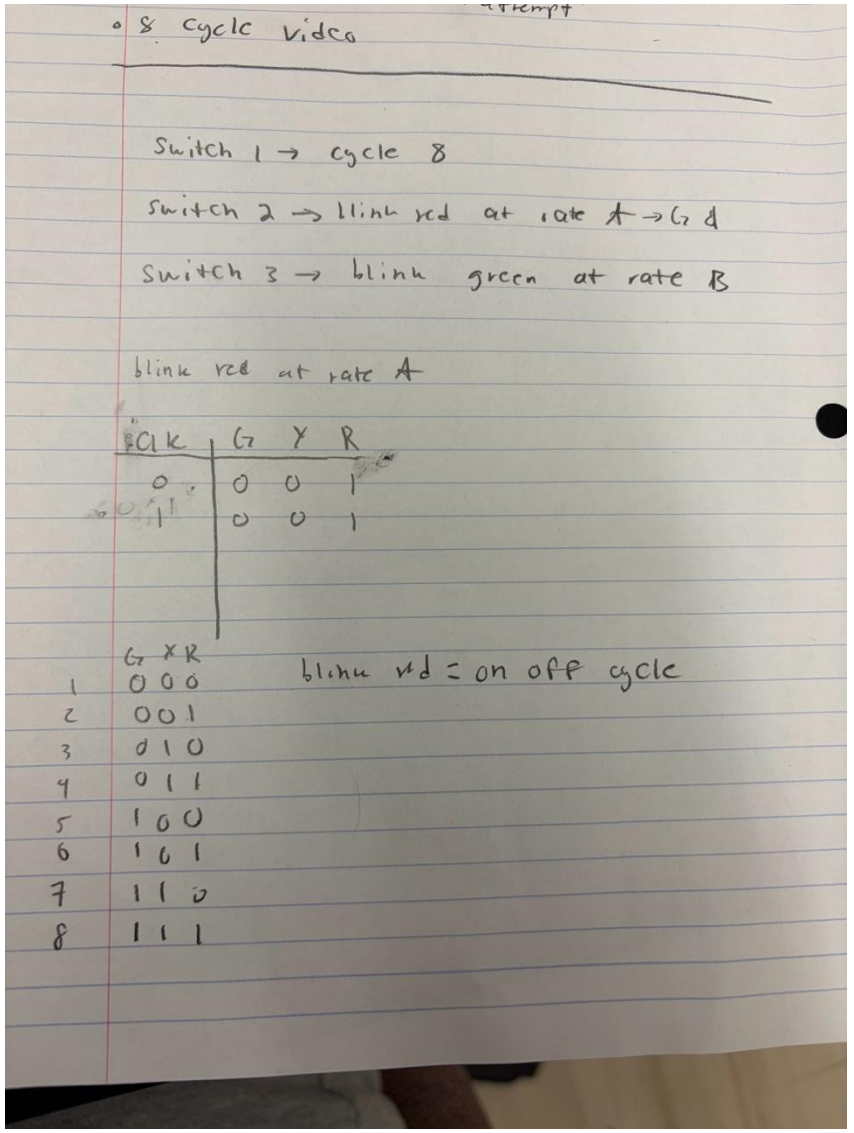

Would have been made nicer for report

Cycle 8 Patterns at 1 sec rate

Truth Table

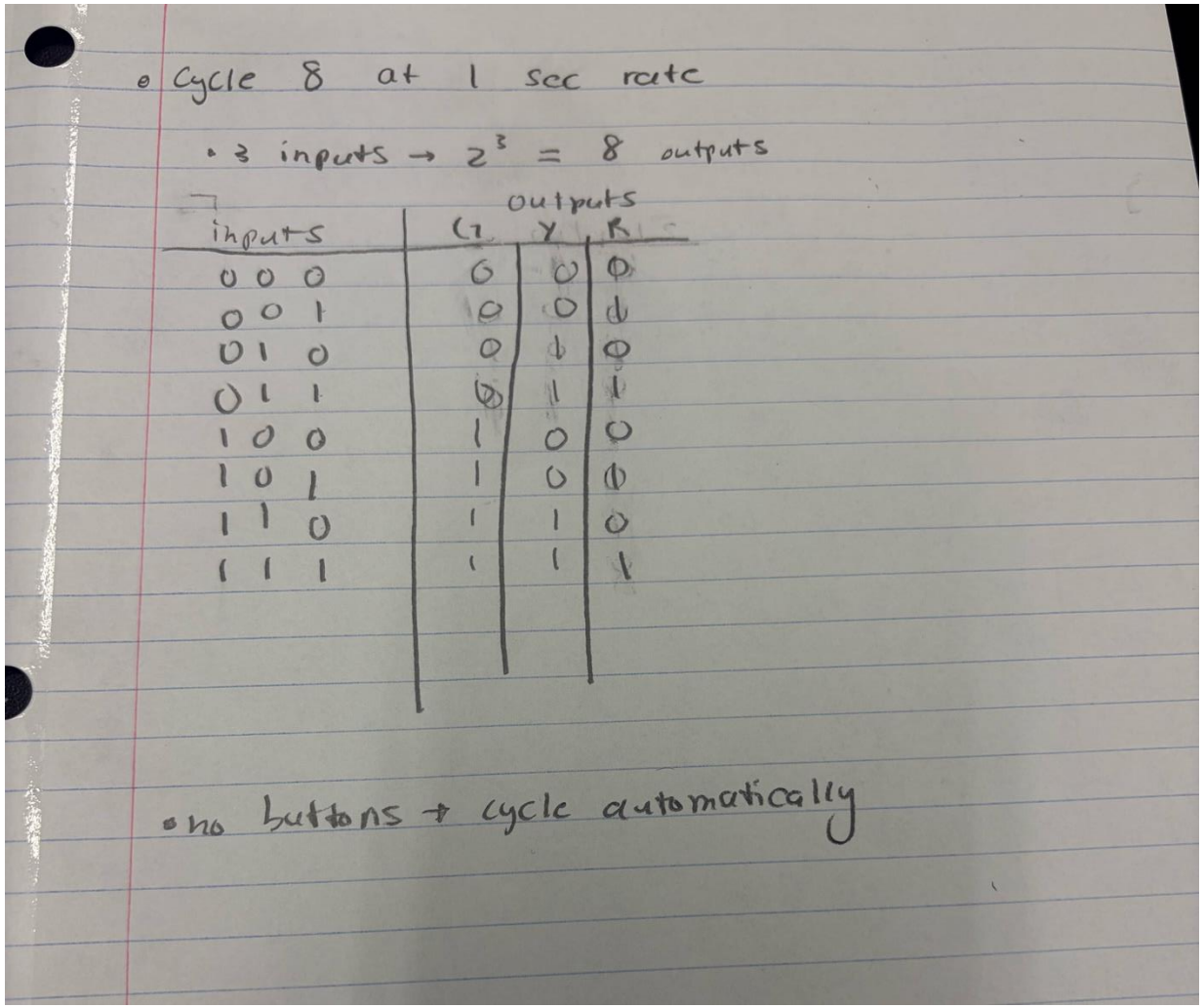


- Cycle 8 at 1 sec rate
  - 3 inputs → $2^3 = 8$ outputs

inputs	outputs		
	G	Y	R
0 0 0	0	0	0
0 0 1	0	0	1
0 1 0	0	1	0
0 1 1	0	1	1
1 0 0	1	0	0
1 0 1	1	0	1
1 1 0	1	1	0
1 1 1	1	1	1


- no buttons → cycle automatically

Trial 1

Thinking I could have different states that it rotates through for each pattern, but quickly realized that might not be the best approach

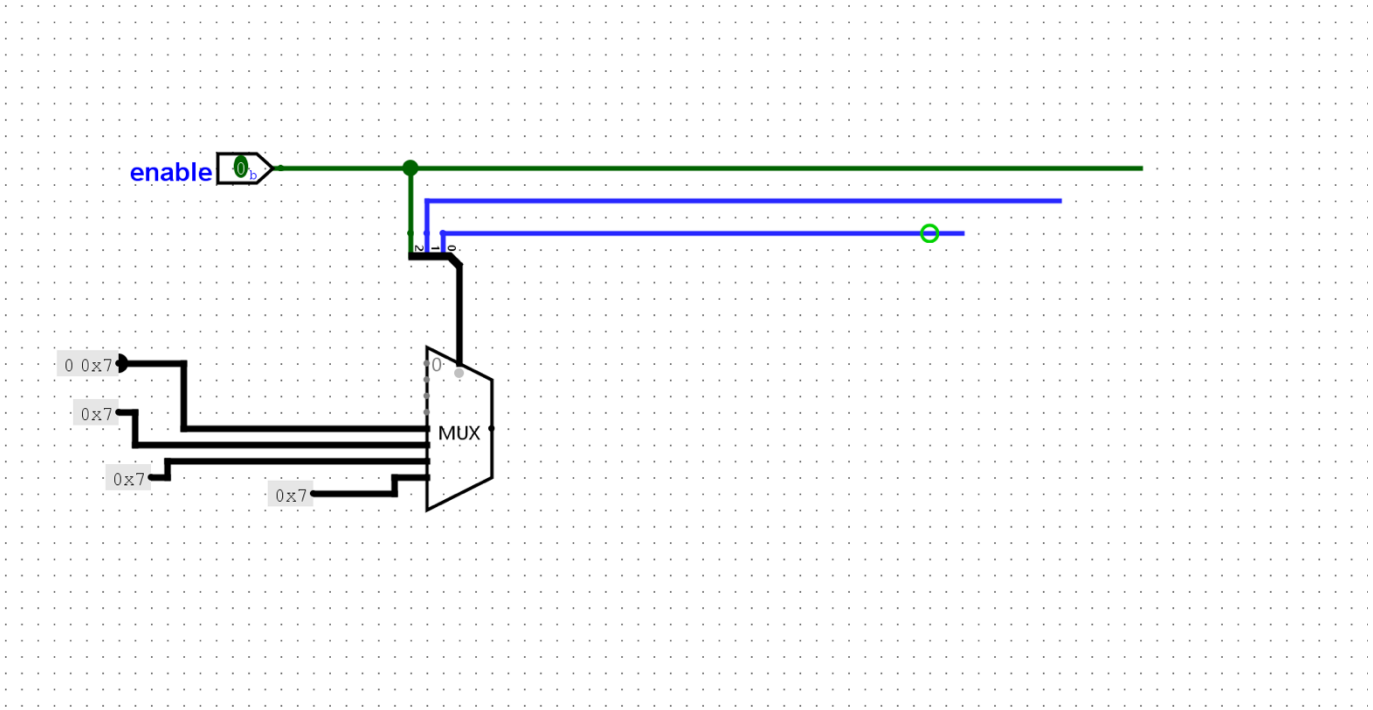


Trial 2: success

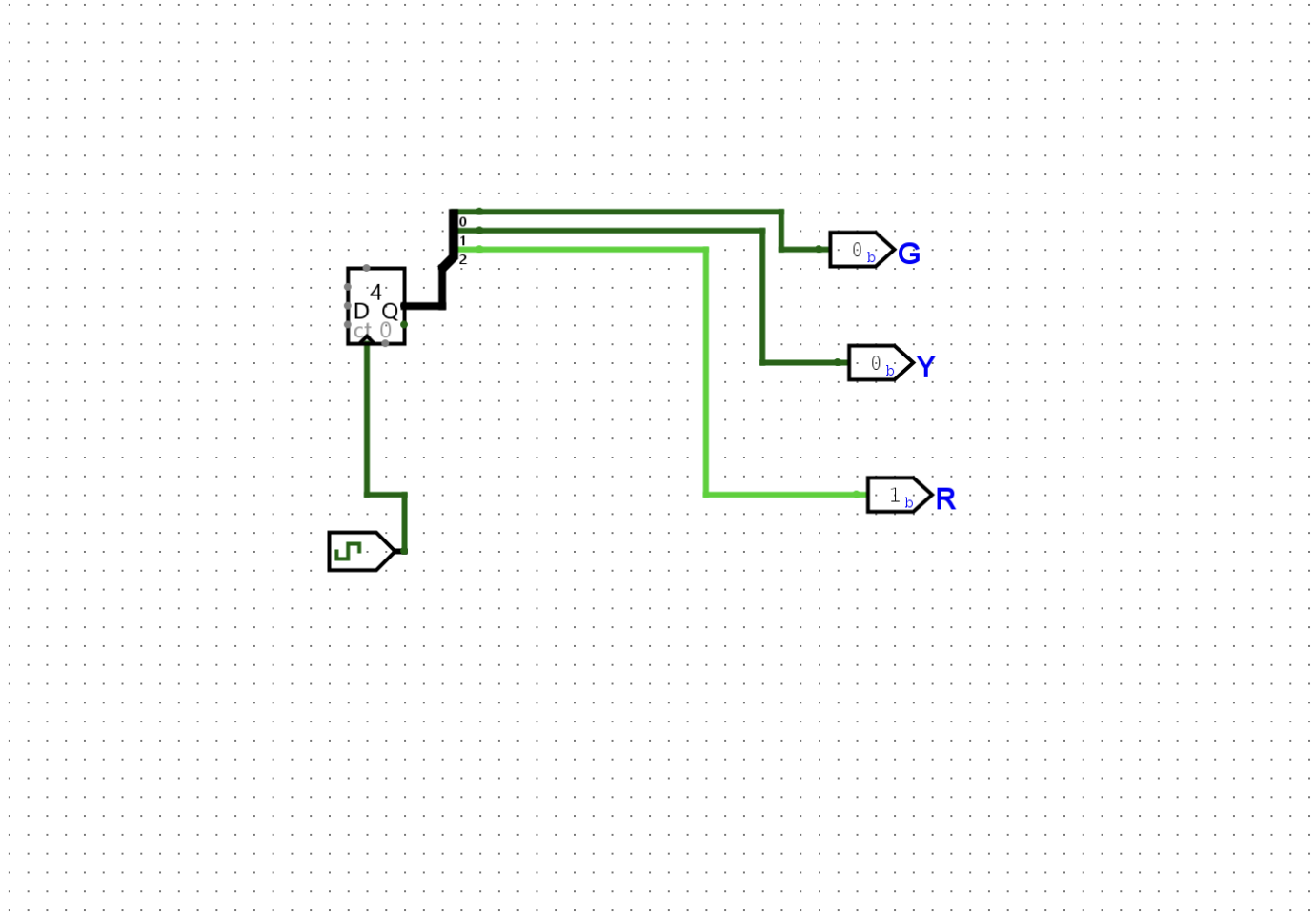

Cycle 8 + Red at Rate A + Green at Rate B

Trial 1

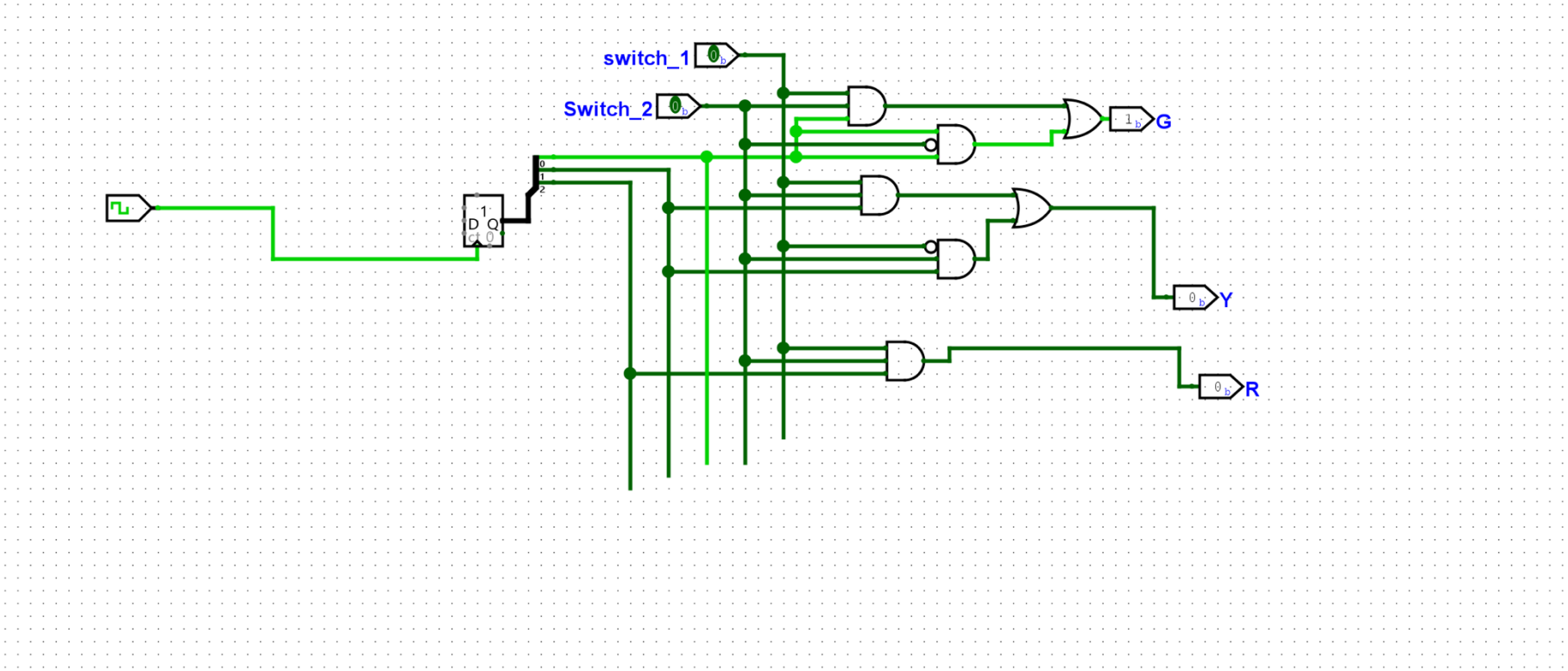Mostly worked but needed both switches on for one condition to cue



Possible Solution

Worked but accidentally had blue blink instead of red

