
Lab 7


Grace Dreiling

Down-counter from 3-0

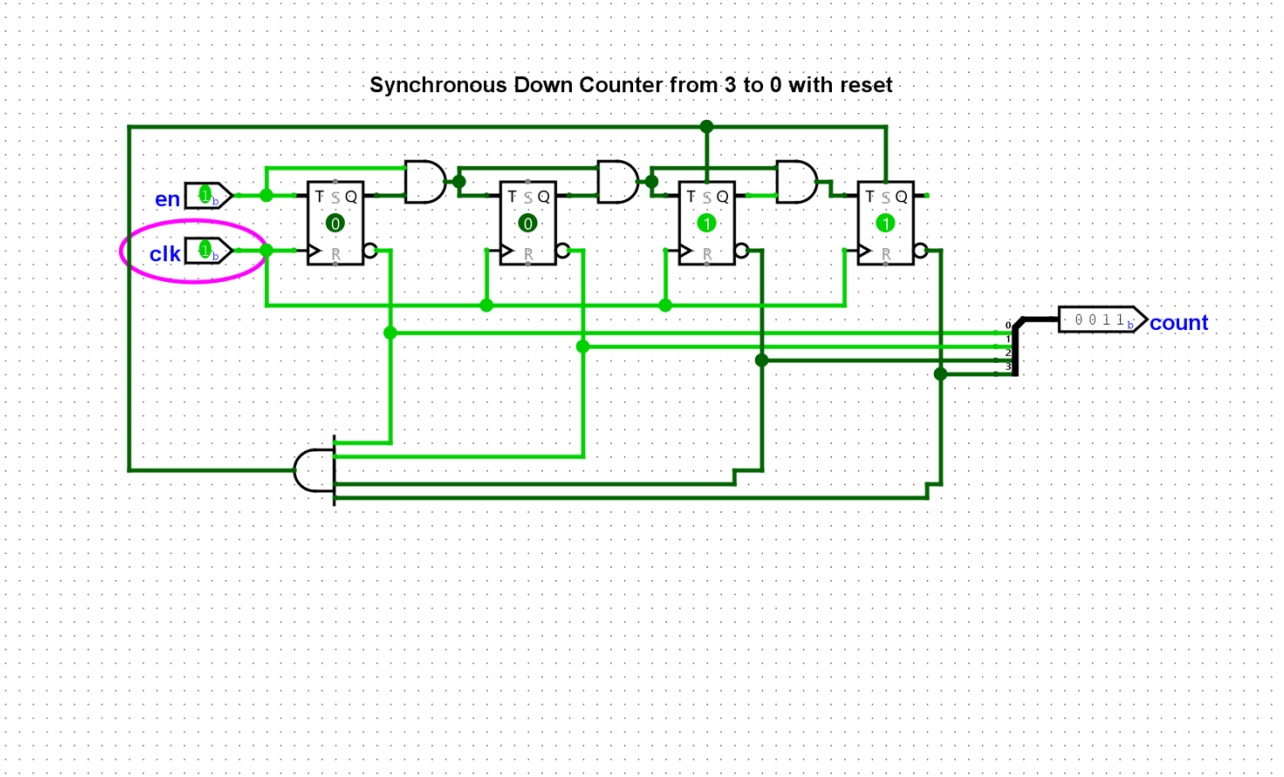
Set the counter set pins to the complement of 3 in order to set the timer to go from 3-0




Drawing of FSM: Before Solution

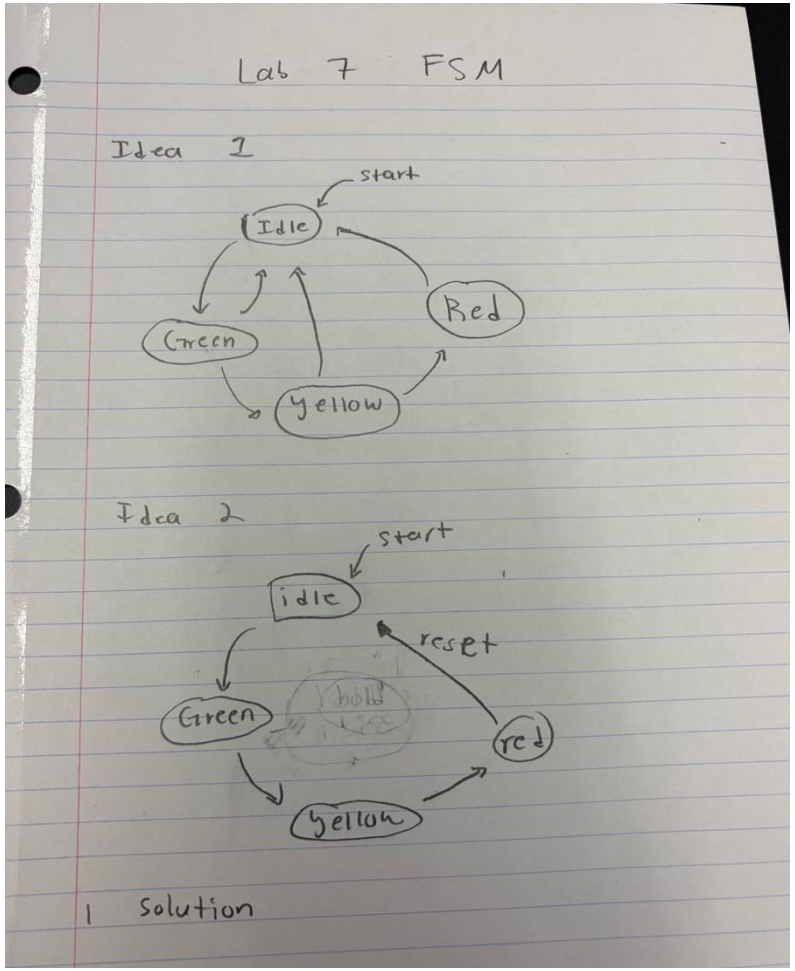

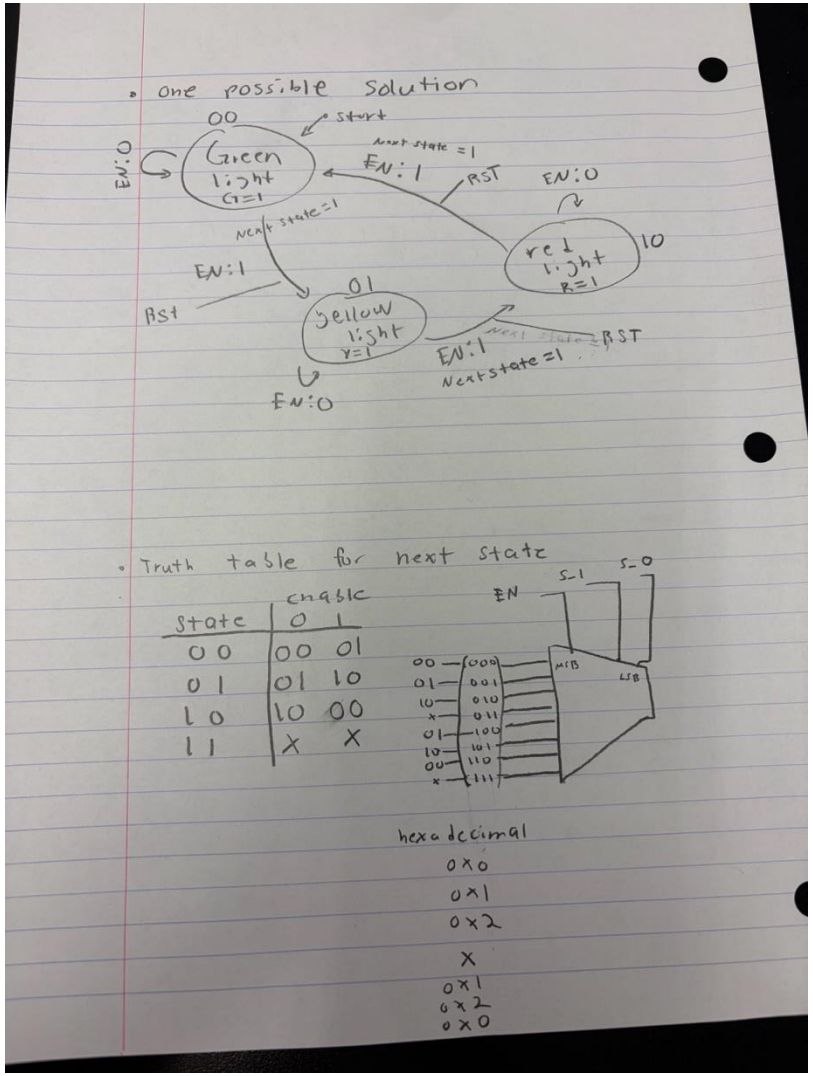
Drawing of FSM: After Solution + Truth Table for Next State




FSM Logic Circuit

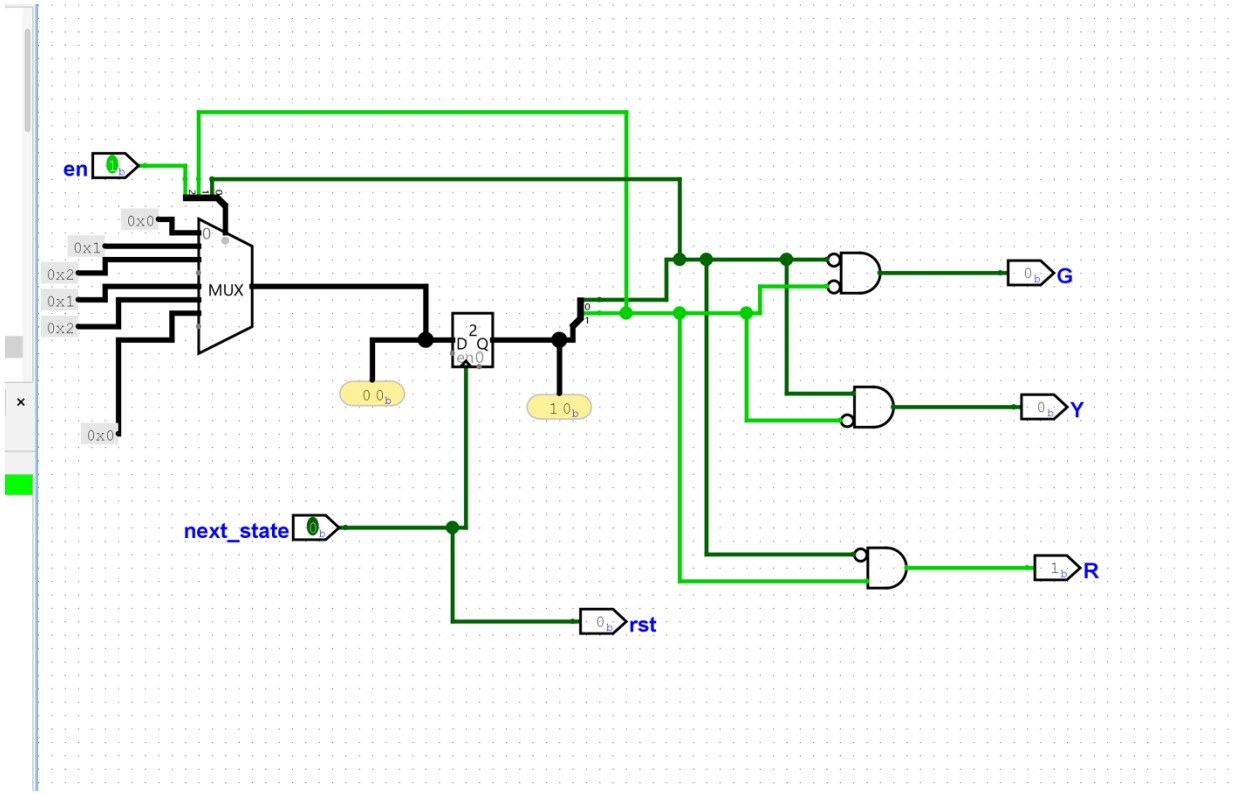

Final Circuit-Yellow

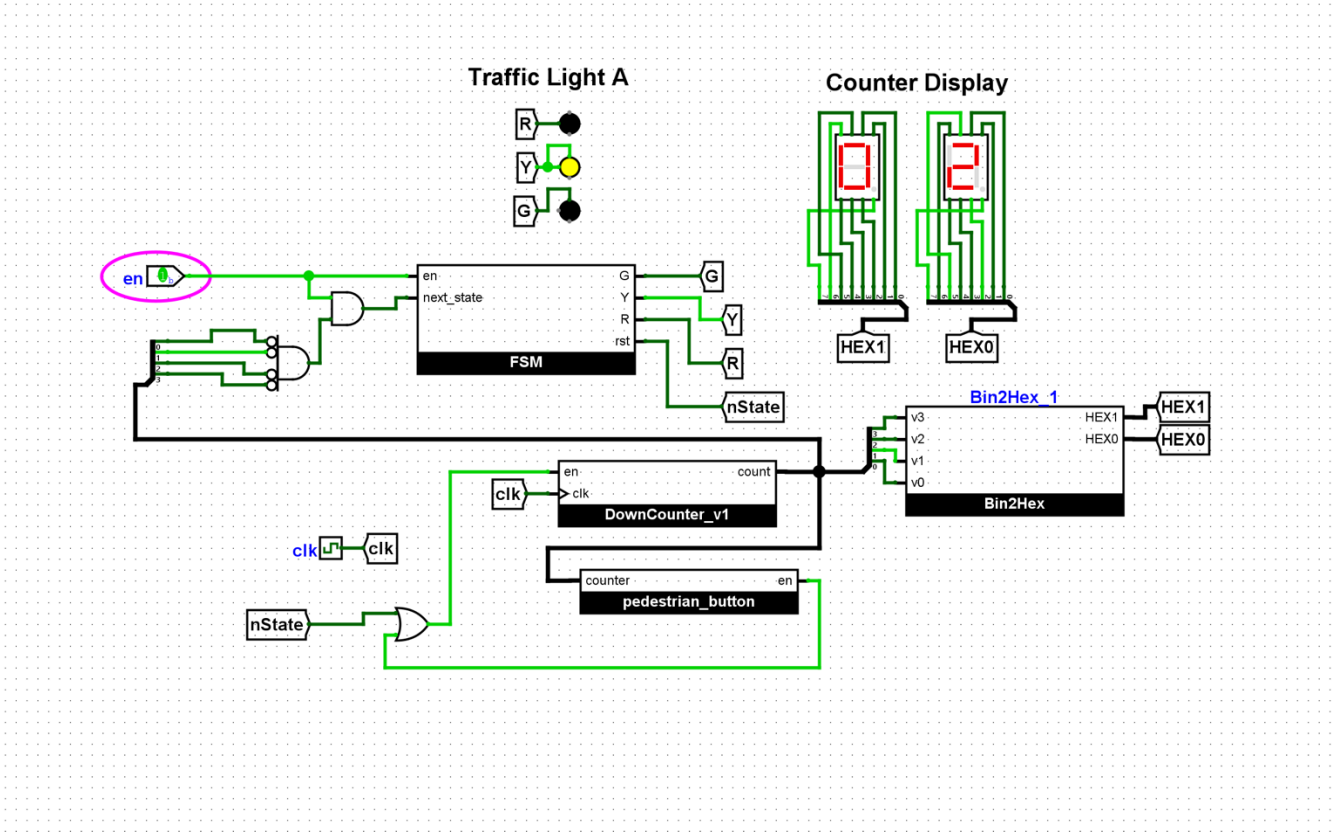

Final Circuit-Green

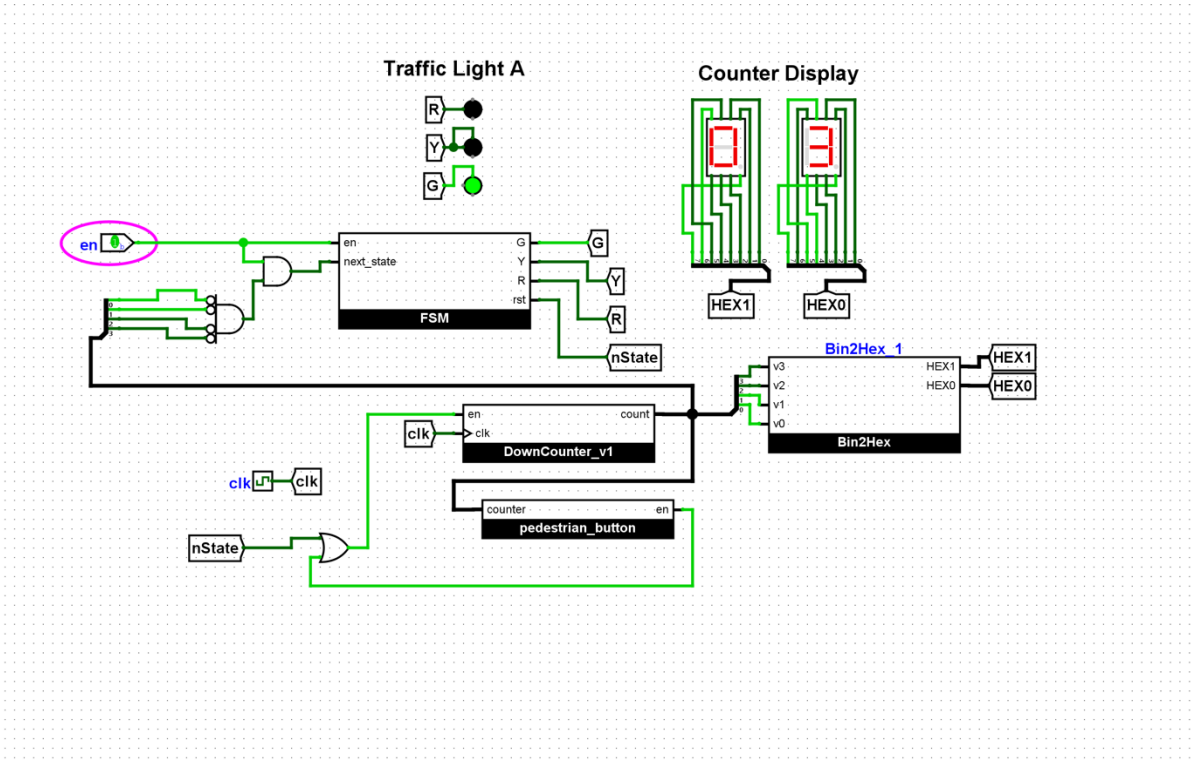

Final Circuit-Red

